

Website:- <https://www.arjun00.com.np>

Council for Technical Education and Vocational Training

Office of the Controller of Examinations

Sanothimi, Bhaktapur

Regular/Back Exam-2078, Magh/Falgun

Program: Diploma in Computer Engineering

Full Marks:80

Year/ Part: I/II (2018)

Pass Marks: 32

Subject: Digital Logic

Time: 3 hrs.

Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full marks.

Attempt Any Five Questions.

1. a) Differentiate analog and digital signals. What do you mean by positive and negative logic. [6+2]
b) Perform following task : [4x2]
 - i Convert $(41.6875)_{10}$ into binary
 - ii Convert $(1001)_2$ into BCD
 - iii Convert $(1011)_2$ into decimal
 - iv Convert $(12AB)_{16}$ into decimal
2. a) Explain about basic gates with necessary truth table and logical expression. [8]
b) Explain universal gates and why are they called so? [2+6]
Reduce the following expression using k-map.
 $F(A,B,C,D) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
3. a) State and prove De-Morgan theorem using truth table and logic diagram. Subtract $(11101010)_2$ from $(11111000)_2$ using 2's complement. [5+3]
b) Explain the working of 8 to 1 multiplexer with necessary diagram and truth table. What do you mean by combinational logic circuit? Website:- <https://www.arjun00.com.np> [6+2]
4. a) Define Boolean Algebra. State and explain basic properties of Boolean Algebra. [2+6]
b) Design BCD to Decimal decoder with necessary diagram and truth table and mention different types of decoder IC package. [6+2]
5. a) Define latch and flip-flop. Explain JK flip-flop with all necessary diagram ; symbol, truth table. [2+6]
b) Explain Ripple up counter with timing diagram. [8]
6. Write short notes on : **(Any Four)** [4x4=16]
 - i) SISO shift register
 - ii) LCD display
 - iii) 7- Segment Display
 - iv) Half adder
 - v) Alphanumeric code

Good Luck !

Website:- <https://www.arjun00.com.np>