



**Back Exam-2080 Mangsir/Poush (Scholarship)**

**Program: Diploma in Information Technology**

**Full Marks: 80**

**Year/Part: I/II (2016)**

**Pass Marks: 32**

**Subject: Digital Logic**

**Time: 3 hrs.**

*Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full marks.*



[www.arjun00.com.np](http://www.arjun00.com.np)

**Attempt any TEN questions.**

1. Define analog and digital signal in short. Mention the advantages of digital signal over analog signal. [4+4]
2. Explain binary number system. Convert the following: [2+6]
  - i.  $(1011)_2 = (?)_{10}$
  - ii.  $(37)_{10} = (?)_2$
  - iii.  $(BAF)_{16} = (?)_{10}$
3. Explain D-flip flop and T flip flop with their truth table. [4+4]
4. Define shift registers. Explain SISO and SIPO shift registers. [2+6]
5. What are counters? Explain ripple counter. [2+6]
6. What are decoders? Explain 4 to 1 multiplexer and 1 to 4 demultiplexer. [2+3+3]
7. Perform the following: [4×2]
  - i.  $(1000)_2 + (1101)_2$
  - ii.  $(101)_2 - (01)_2$
  - iii.  $(1111)_2 \div (101)_2$
  - iv.  $(1011)_2 \times (101)_2$
8. What do you mean by logic families? Introduce TTL, ECL and RTL families in short. [2+6]
9. What do you mean by universal gates? Explain the universal properties of NAND gate. [2+6]
10. Minimize the following expression: [8]
$$F = \sum m(0, 7, 8, 9, 10, 12) + \sum d(2, 5, 13); \text{ using k-map.}$$
11. Differentiate combinational and sequential logic circuit with example. Explain 7-segments display. [4+4]
12. Write short notes on: (any TWO) [2×4]
  - a. Full Adder
  - b. SOP and POS
  - c. Alphanumeric Code
  - d. Master Slave JK flip flop



[www.arjun00.com.np](http://www.arjun00.com.np)

**Good Luck !**