



Regular/Back Exam-2079, Phagun/Chaitra

Program: Diploma in IT Engineering

Full Marks: 80

Year/Part: I/II (2016)

Pass Marks: 32

Subject: Digital Logic

Time: 3 hrs.

© Arjun

Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full marks.

Attempt any **FIVE** questions.



www.arjun00.com.np

1. a) Define signal. Differentiate between analog and digital signal [1+3]
with suitable example.
- b) Convert the following number system: [4×2]
 - i. $(2567.350)_{10} = (?)_2$
 - ii. $(BCDE.4A)_{16} = (?)_8$
 - iii. $(1100110011)_2 = (?)_{16}$
 - iv. $(376.351)_8 = (?)_{10}$
- c) Perform the following operation: [2×2]
 - i. Divide: $(1100110011)_2 / (1011)_2$
 - ii. Multiply: $(1011001101)_2 \times (101101)_2$
2. a) State and prove De-Morgan's Theorem with necessary [8]
diagram and truth table.
- b) Simplify the following expression using Boolean Algebra. [2×4]
 - i. $Z(Y + Z)(X + Y + Z) = Z$
 - ii. $A'BC + AB'C + ABC + BC'$
3. a) Simplify the following expression using k-map. [2×4]
 - i. $\sum F(A, B, C, D) = \pi m(2, 3, 4, 5, 7, 10, 11, 14) + \sum d(0, 1, 6, 15)$
 - ii. $\sum F(A, B, C, D) = \sum M(0, 1, 4, 8, 11, 12, 15) + \sum d(2, 3, 5, 7)$
- b) Realize basic gate using universal NAND gate only with [8]
truth table and logic circuit.
4. a) Define multiplexer. Explain the operation of full subtractor [2+6]
with clear logic diagram, truth table and expression.

Cont.....

- b) Define encoder. Design and explain seven segment Display decoder with necessary diagram and truth table. [2+6]
5. a) Define counter. Explain the operation of 'T' flip flop with necessary diagram and truth table. [2+6]
- b) Define adder. Explain about ripple counter with necessary diagram. [2+6]
6. Write short notes on: (Any Four) [4×4]
- a) ASCII Code
 - b) DTL Logic Family
 - c) AND & OR Gates
 - d) 1:4 De-multiplexer
 - e) SISO Shift Register

Good Luck!



www.arjun00.com.np

AC