



Program: Diploma in Information Technology/
Computer Engineering

Full Marks: 80

Year/Part: II/I (2022)

Pass Marks: 32

Subject: Digital Logic

Time: 3 hrs.

Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full marks.

Attempt any **FIVE** questions. www.arjun00.com.np

1. a. Define signal. Differentiate between analog and digital signal [1+3]
with suitable example.
b. Convert the following number system: [4×2]
 - i. $(10111.01)_2 = (?)_{10}$
 - ii. $(3471)_8 = (?)_{16}$
 - iii. $(BCDE.4A)_{16} = (?)_8$
 - iv. $(3567.350)_{10} = (?)_2$
- c. Perform the following operation: [2×2]
 - i. Multiply: $(11101.11 \times 101)_2$
 - ii. Divide: $(110100.110 / 110)_2$
2. a. Subtract the following $(11001100)_2$ from $(11110000)_2$ using [4]
2's complement.
b. Realize basic gate using NAND gate only with clear diagram [4+4]
and truth table. Also, state and prove De-Morgan's Theorem
in brief.
c. Explain XOR and NOR gate with truth table and symbol. [4]
3. a. Simplify the following expression using Boolean algebra: [4×2]
 - i. $A'B'C' + A'BC' + AB'C' + ABC' = C'$
 - ii. $A(A' + C)(A'B + C)(A'BC + C') = 0$
- b. Simplify the following expression using k-map. [4×2]
 - i. $\sum f(A, B, C, D) = \pi M(2, 3, 4, 5, 7, 10, 11, 14) + \sum d(0, 1, 6, 15)$
Draw logic diagram.
 - ii. $\sum f(A, B, C, D) = \sum m(0, 1, 4, 8, 11, 12, 15) + \sum d(2, 3, 5, 6, 7)$
Draw logic diagram. www.arjun00.com.np
4. a. Define encoder. Explain the decimal to binary encoder with [2+6]
suitable diagram and truth table.

- b. Differentiate between combinational and sequential circuit [4]
with example.
- c. Design 1:4 De-multiplexer with clear circuit diagram and [4]
truth table in brief.
5. a. Design RS flip-flop with necessary diagram. Write the [6+2]
advantages of JK flip-flop.
- b. Define shift register. Explain the operation of ripple counter [2+6]
with clear diagram.
6. Write short notes on: (any **FOUR**) [4×4]
- a. 7 segments display
 - b. SIPO shift register
 - c. D flip-flop
 - d. Half adder
 - e. ASCII code
 - f. BCD code

Good Luck !

www.arjun00.com.np

AC